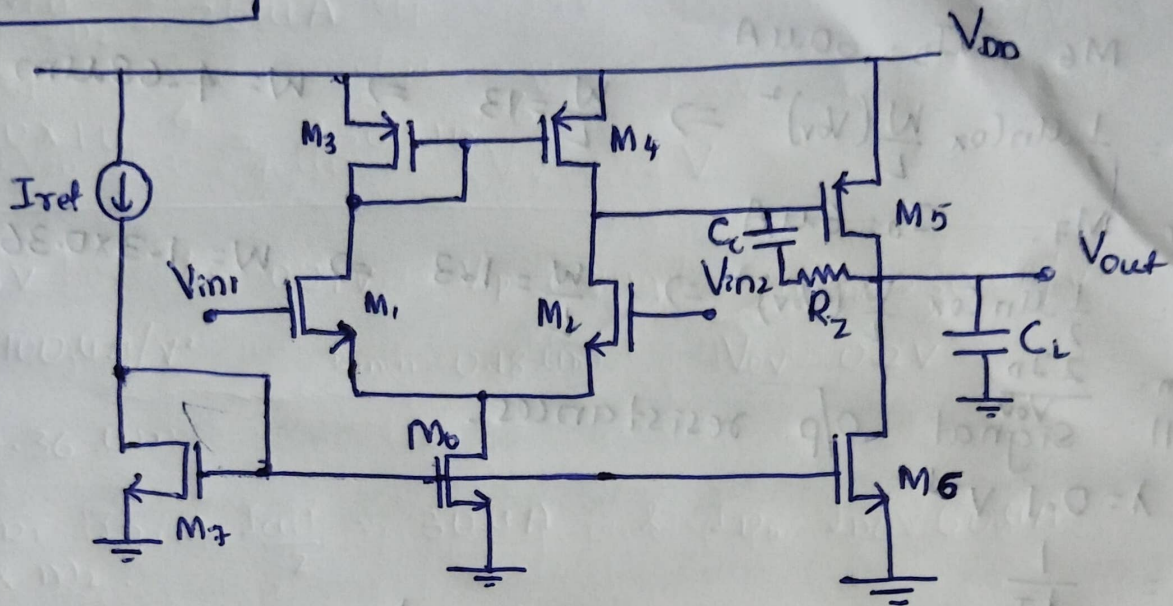


2 stage OTA design

B. Srishanth
240102023



$V_{DD} = 1.8V$, $\mu_{n}C_{ox} = 230 \mu A/V^2$, $\mu_{p}C_{ox} = 100 \mu A/V^2$, $V_{ov} = 0.2V$
 $V_{tn} = 0.37V$, $V_{tp} = 0.39V$, $L_{min} = 0.18 \mu m$, $W_{min} = 0.27 \mu m$
 $C_L = 10pF$, $C_c \geq 0.22 pF$, SO, $C_c = 10pF$ & $R_z = 2K$
 Let $L = 0.36 \mu m$ & $I_{ref} = 6 \mu A$

$I_{tail} = 10 \cdot I_{ref} = 60 \mu A \Rightarrow I_{D1} = I_{D2} = 30 \mu A$
 and Also, take $I_{D5} = I_{D6} = 60 \mu A$.

For M_1 & M_2 , $I_D = 30 \mu A$

$$I_D = \frac{1}{2} \mu_{n} C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 6.52 \Rightarrow W = 6.52 \times 0.36 = 2.35 \mu m$$

$$g_m = \frac{2I_D}{V_{ov}} = 300 \mu S$$

For M_5 , $I_D = 60 \mu A$.

$$I_D = \frac{1}{2} \mu_{n} C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 13.0 \Rightarrow W = 13 \times 0.36 = 4.68 \mu m$$

$$g_m = \frac{2I_D}{V_{ov}} = 600 \mu S$$

For M_3 & M_4 , $I_D = 30 \mu A$

$$I_D = \frac{1}{2} \mu_{p} C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 15 \Rightarrow W = 15 \times 0.36 = 5.4 \mu m$$

$$g_m = \frac{2I_D}{V_{ov}} = 300 \mu S$$

For M_5 , $I_D = 60 \mu A$

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 30 \Rightarrow W = 30 \times 0.36 = 10.8 \mu m$$

$$g_m = \frac{2I_D}{V_{ov}} = 600 \mu S$$

For M_6 , $I_D = 60 \mu A$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 13 \Rightarrow W = 4.68 \mu m$$

For M_7 , $I_D = 6 \mu A$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{ov})^2 \Rightarrow \frac{W}{L} = 1.3 \Rightarrow W = 1.3 \times 0.36 \approx 0.47 \mu m$$

$$g_m = \frac{2I_D}{V_{ov}}$$

Small signal o/p resistances.

$$\text{at } \lambda = 0.1 V^{-1}$$

$$r_o = \frac{1}{\lambda I_D}$$

$$\text{So, For } M_1, M_2, M_3, M_4 \Rightarrow r_o = \frac{1}{0.1 \times 30 \mu A} \approx 333 k\Omega$$

$$\text{For } M_5, M_6, M_0 \Rightarrow r_o = \frac{1}{0.1 \times 60 \mu A} \approx 167 k\Omega$$

$$\text{For } M_7 \Rightarrow r_o = \frac{1}{0.1 \times 6 \mu A} = 1670 k\Omega$$

Theoretical gain.

Stage-1

$$A_{v1} = g_{m1} (r_{o1} || r_{o3}) = 300 \mu \times 160 k = 49.8$$

Stage-2

$$A_{v2} = g_{m2} (r_{o5} || r_{o6}) = 600 \mu \times 83 k = 49.8$$

Total gain

$$A_v = A_{v1} \times A_{v2} = ~~49.8 \times 49.8~~ 49.8 \times 49.8 = 2480$$


$$A_v (\text{in dB}) = 20 \log(2480) \approx 67.89 \text{ dB}$$

Power consumption:

$$I_{\text{total}} = 60 \mu + 60 \mu = 120 \mu A$$

$$P = 1.8 \times 120 \mu = 216 \mu W$$

closed loop.

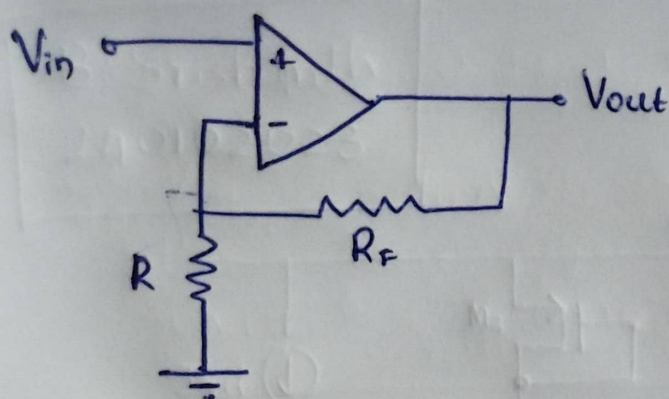

Let $R = R_f = 100k$

$$\text{Gain} = 1 + \frac{R}{R_f} = 2$$

$$\text{Gain (in dB)} = 20 \log(2) = 6.02 \text{ dB}$$

From Experiment:-

(i) Open loop circuit configuration

• Experimental gain = 64.59 dB (at 1 kHz)

• Phase Margin = $180 - 121.687 = 58.313^\circ$

(ii) Closed loop circuit configuration (for DC gain 2)

• Experimental gain = 6.015 dB

• ~~Phase~~ phase margin = $180 - 101.107 = 78.893^\circ$

Table

	g_m	r_o	I_D	$V_{GS} - V_T$	$L(\text{in } \mu\text{m})$	$W(\text{in } \mu\text{m})$
M_0	600 μs	167 k Ω	60 μA	0.206	0.36	2.35
M_{1-2}	300 300 μs	333 k Ω	30 μA	0.23	0.36	4.68
M_{3-4}	300 μs	333 k Ω	30 μA	0.21	0.36	5.4
M_5	600 μs	167 k Ω	60 μA	0.21	0.36	10.8
M_6	600 μs	167 k Ω	60 μA	0.23	0.36	4.68
M_7	60 μs	1670 k Ω	6 μA	0.206	0.36	0.47